# Logic

#### Digital electronics

9/6/2023

## 1 Binary Codes

Binary Code is how information is represented with binary digits, mulitple exist. Codes provide further implementation methods of binary into a digital system.

**Binary Coded Decimal** is code to represent decimal in binary. Each digit is represented by its binary 4-bit equivalent.

Application include numeric LED displays. (BCD is translated digit by digit and the appropriate number is shown)





### Logic

Logic math (Boolean Algebra) existed before digital computers. It explained logic, by the means of math, utilizing 2 values (*True or False*).

- As a transistor is a binary output, logic can be implemented
- Basic functions are AND, OR, NOT
- AND  $\rightarrow$ All inputs mus the true for the expression too be true. z = xy, z = x \* y
- OR  $\rightarrow$  Any 1 input can be true for the expression to be true. z = x + y
- NOT  $\rightarrow$ Reverse the expression/scoped output from true to false and vice versa.  $z = x' = \bar{x}$


**Truth Tables of Logical Operations** 

AND			OR			NOT	
х	у	$x \cdot y$	х	y	x + y	х	x'
0	0	0	0	0	0	0	1
0	1	0	0	1	1	1	0
1	0	0	1	0	1		
1	1	1	1	1	1		
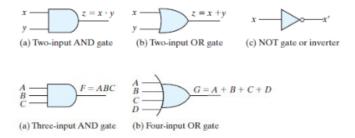
### Logic gates

These functions are implemented with logic gates, Electronic device to implement Boolean function.

- These gatees have mulitple inputs and one output.
- They use specific symbols in their schematic representation



#### **Boolean Functions**

Varibales are used to represent inputs and outputs. in a Boolean function, ANDs appear as a product and ORs appear as a sum. NOT is represented with a ' or a bar above the variable.

