


# Comparators, Multiplexers

---
 
# Multiplexers

---

- \* Directs one of multiple inputs to a single output
- \* Select lines determine what input is switched to the output. Passes an input to output
- \* Max # of inputs =  $2^n$ , where  $n$  is # of select lines




$S$	$Y$
0	$I_0$
1	$I_1$

# Multiplexer

---

\* 4 inputs need 2 select lines.  $I_3$  is the MSB


$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

 
 
# What's Inside a Multiplexer


---

- \* Law of AND  $\rightarrow A \text{ AND } 1 \text{ is } A$
- \* Law of OR  $\rightarrow A \text{ OR } 0 \text{ is } A$
- \* Select lines are used to activate only one AND gate





# 4 Input

$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

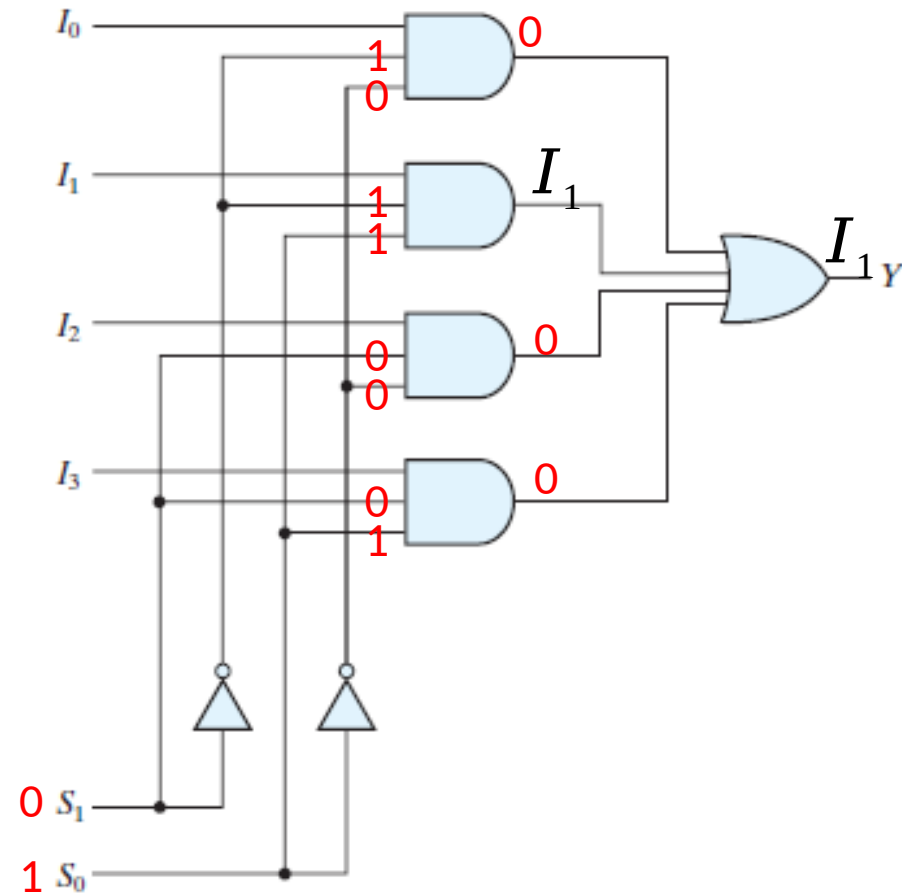
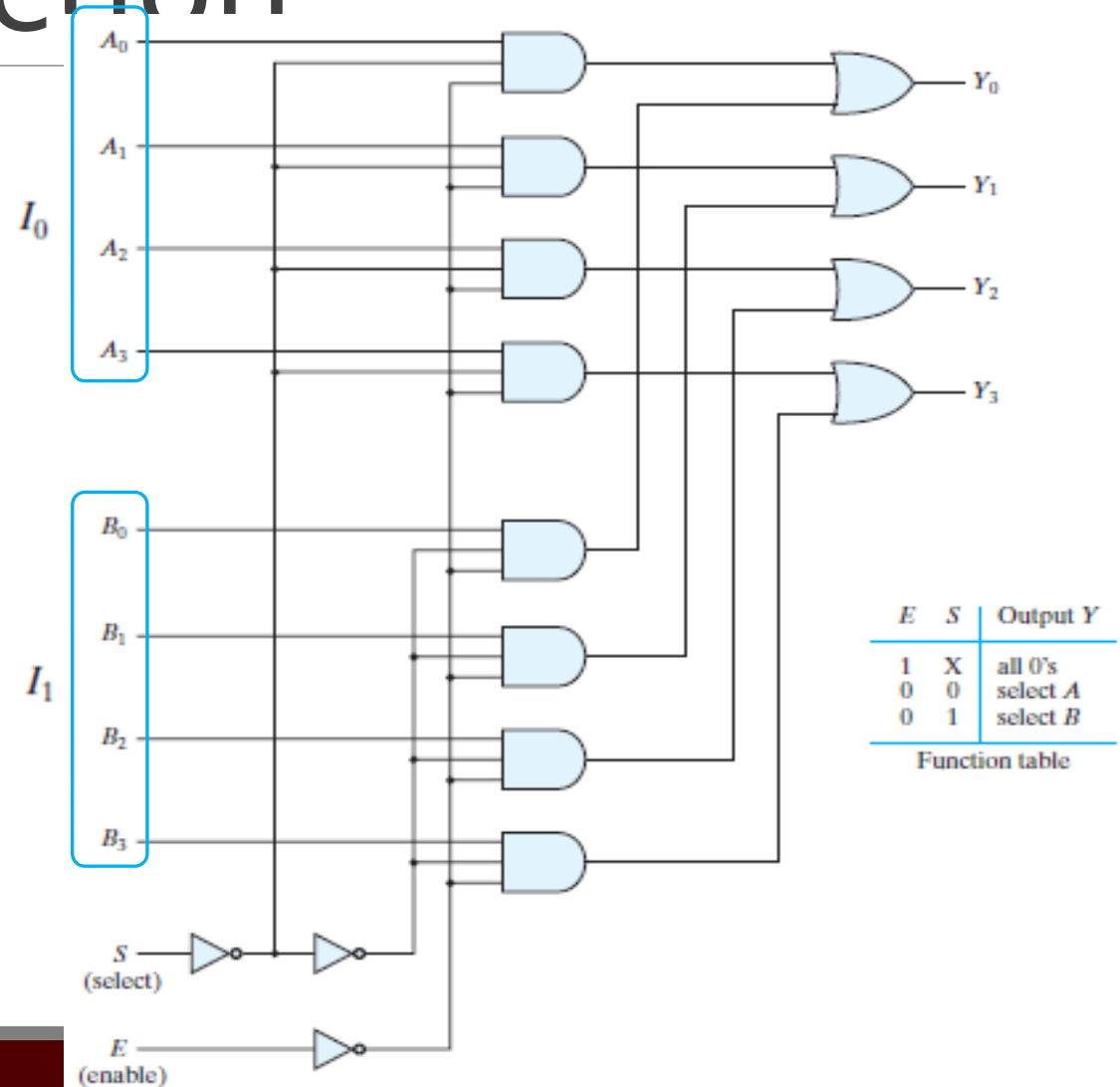 
# Multiple Bit Selection

- \* Multiple bits can be passed to output
- \* Group A is one input of multiple bits
- \* Group B is another input of multiple bits
- \* 1 bit select line with active low enable




# Using Parallel Multiplexers

---

- \* Placing multiplexers in parallel will allow for bus inputs
- \* The # of multiplexers in parallel is the number of bits on each bus input
- \* Each multiplexer will switch one digit of the multiple bit number
 
# Parallel Multiplexer


\* Allows a two 3-bit inputs to be switched to 3 – bit output




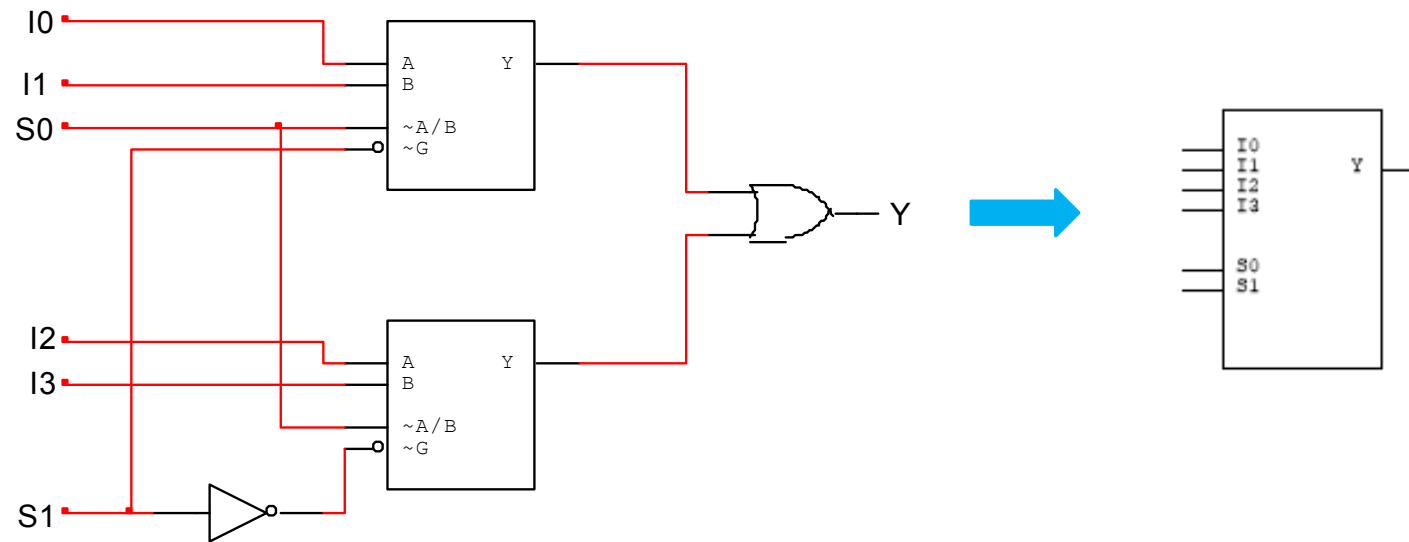
# Cascading Multiplexers

- \* Use enable on multiplexer to create additional select line
- \* Connect remaining select lines together
- \* OR outputs from each multiplexer





$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

# Cascade Multiplexer


\* How would a 4 input multiplexer be cascaded to create a 8 input multiplexer?

S2	S1	S0	Y
0	0	0	I0
0	0	1	I1
0	1	0	I2
0	1	1	I3
1	0	0	I4
1	0	1	I5
1	1	0	I6
1	1	1	I7

  

# Cascade Multiplexer

---

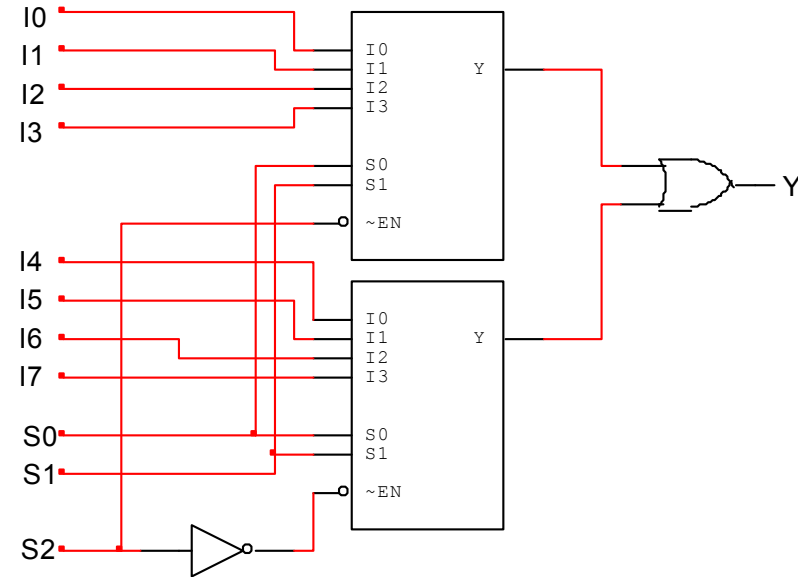

# Implement Combinational Logic Circuits

---

- \* Multiplexers can implement outputs of truth table
- \* One multiplexer for each output
- \* The number of select lines on a multiplexer is number of inputs - 1
  - LSB will be input to multiplexer
  - Remaining bits will be inputs to the select lines
  - 3 input truth table uses 2 select lines which is a 4 input multiplexer
- \* Divide truth table in groups of 2, and compare how LSB changes to output. That becomes input to multiplexer

# Example


---

Implement truth table with multiplexer

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

# Example


---

 
 
# Demultiplexer

---


- \* Directs one input to one of multiple output lines
- \* Number of max outputs is  $2^n$ , where n is # of select lines



A	B	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1
 
# What's Inside a Demultiplexer

\* AND gates to pass input to an output. NOT gates for select lines



$S_0$	$S_1$	$D_0$	$D_1$	$D_2$	$D_3$
0	0	D	0	0	0
0	1	0	D	0	0
1	0	0	0	D	0
1	1	0	0	0	D



# Multiplexer & Demultiplexer Uses

---

- \* Communication systems
- \* Microcontroller peripherals and functions
- \* Signal routing between destinations
- \* Switching functions in electronics

# Comparator


---

- \* Logic device that compares two numbers (A and B) and determines the following:
  - $A = B$
  - $A < B$
  - $A > B$
- \* N – bit comparator
  - N is number of bits in each number to compare

# Making a 1-Bit Comparator

Truth table of 1-bit comparator

A	B	A = B	A < B	A > B
0	0	1	0	0
0	1	0	1	0
1	0	0	0	1
1	1	1	0	0

 

1-bit comparator circuit

# Cascading 1-Bit Comparator


---

- \* Cascading two 1-bit comparators will make a 2-bit comparator
- \* One comparator will compare the MSB bits and the other the LSB bits


# Possible Scenarios

A1	B1	A0	B0	
0	0	0	0	A=B
0	1	1	1	A<B
1	1	0	1	A<B
1	0	0	0	A > B
0	0	1	0	A > B

MSB
LSB

 


# 2-Bit Comparator

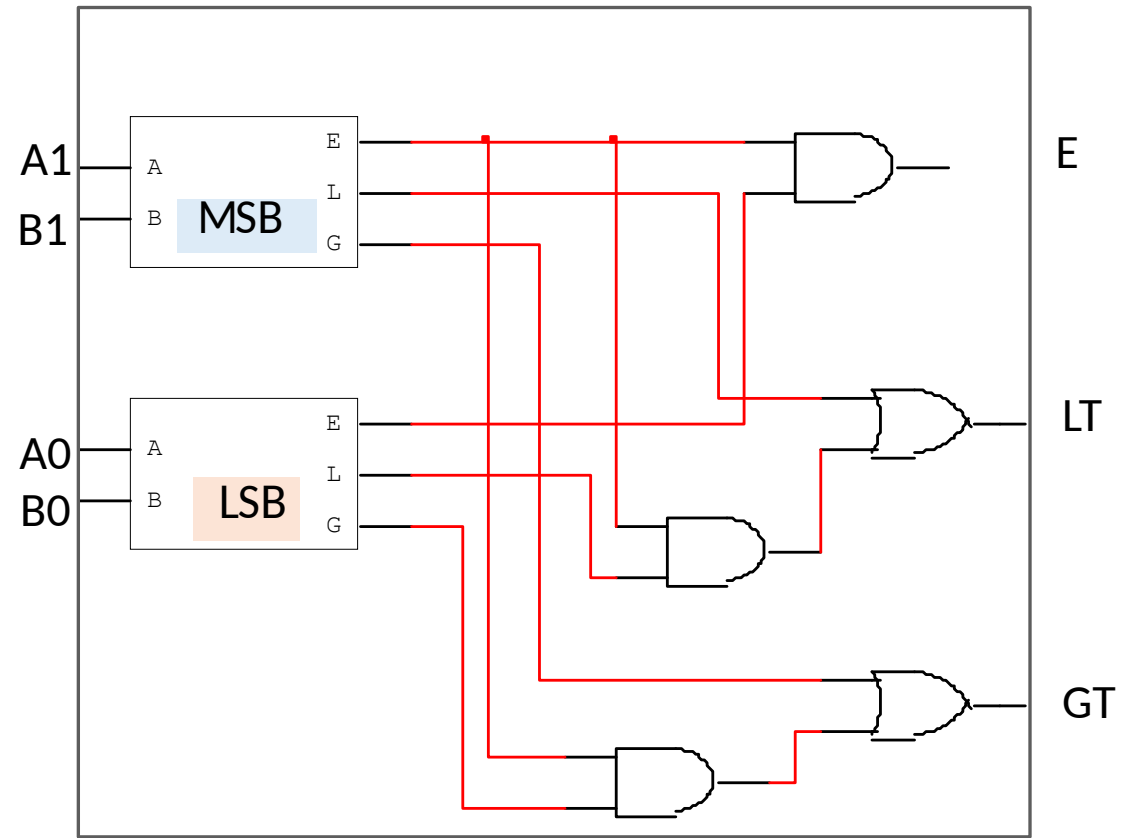

 
# 3 – Bit Comparator

Design a 3-bit comparator using 1-bit comparators



# 3 – Bit Comparator

 



# Making a 2-bit Comparator

A1	A0	B1	B0	A = B	A < B	A > B
0	0	0	0	1	0	0
0	0	0	1	0	1	0
0	0	1	0	0	1	0
0	0	1	1	0	1	0
0	1	0	0	0	0	1
0	1	0	1	1	0	0
0	1	1	0	0	1	0
0	1	1	1	0	1	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	1	0	0
1	0	1	1	0	1	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	1	0	0

		B1B0			
		00	01	11	10
A1A0	00	1			
	01		1		
	11			1	
	10				1

A = B

# 2 – bit Comparator

---



		B1B0			
		00	01	11	10
A1A0	00				
	01	1			
	11	1	1		1
	10	1	1		

$A > B$


		B1B0			
		00	01	11	10
A1A0	00		1	1	1
	01			1	1
	11				
	10			1	

$A < B$

# 2 – bit Comparator

  

# Cascading to make 4-bit

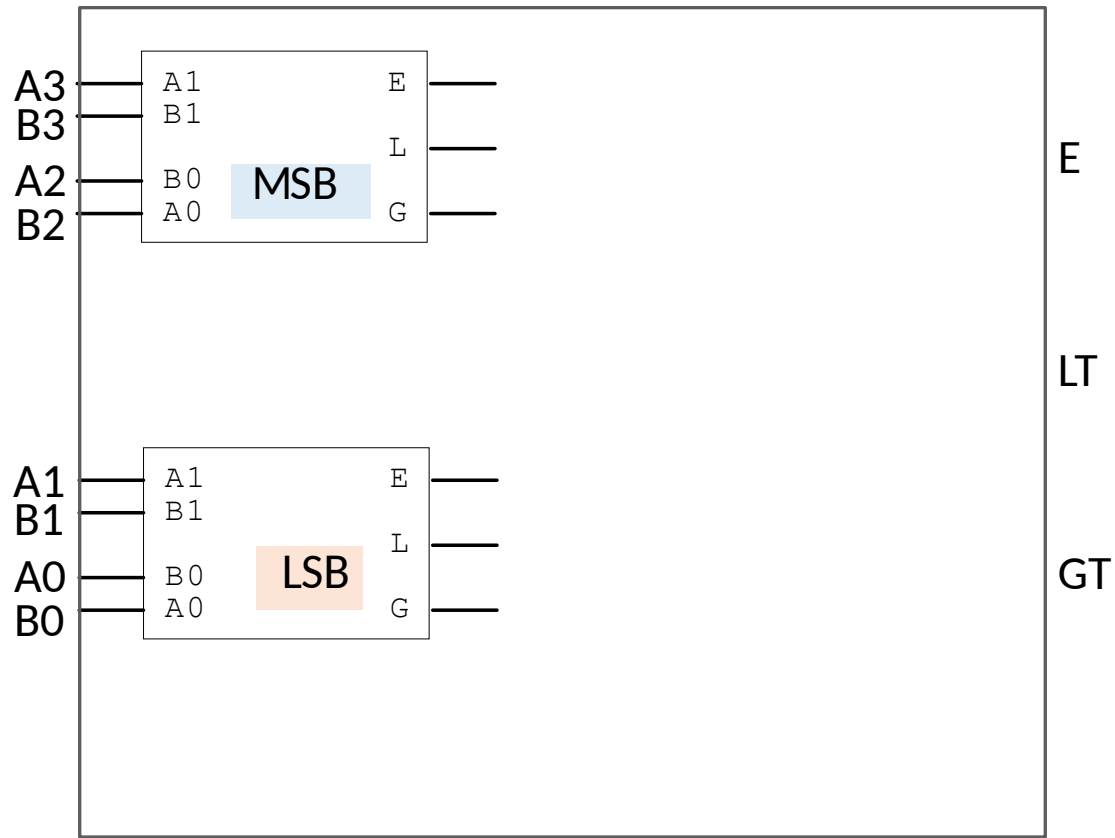

The condition for  $A < B$  can be possible in the following four cases:

If  $A_3 = 0$  and  $B_3 = 1$

If  $A_3 = B_3$  and  $A_2 = 0$  and  $B_2 = 1$

If  $A_3 = B_3$ ,  $A_2 = B_2$  and  $A_1 = 0$  and  $B_1 = 1$

If  $A_3 = B_3$ ,  $A_2 = B_2$ ,  $A_1 = B_1$  and  $A_0 = 0$  and  $B_0 = 1$

The condition of  $A > B$  can be possible in the following four cases:

If  $A_3 = 1$  and  $B_3 = 0$



If  $A_3 = B_3$  and  $A_2 = 1$  and  $B_2 = 0$

If  $A_3 = B_3$ ,  $A_2 = B_2$  and  $A_1 = 1$  and  $B_1 = 0$

If  $A_3 = B_3$ ,  $A_2 = B_2$ ,  $A_1 = B_1$  and  $A_0 = 1$  and  $B_0 = 0$

# Comparator Schematics



\* 4 – bit comparator

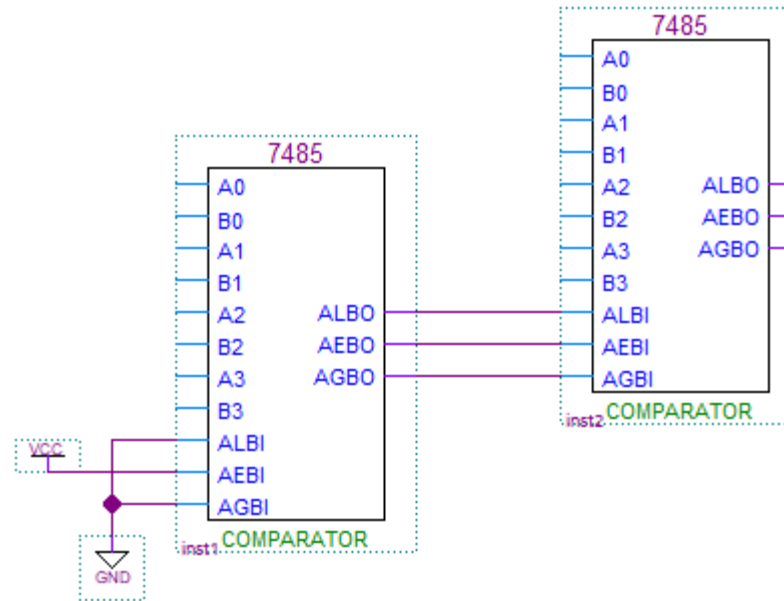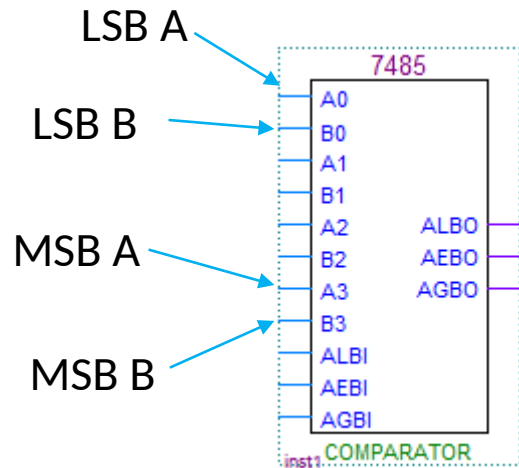

Cascading Comparators


# Comparator Schematics

\* 4 – bit comparator

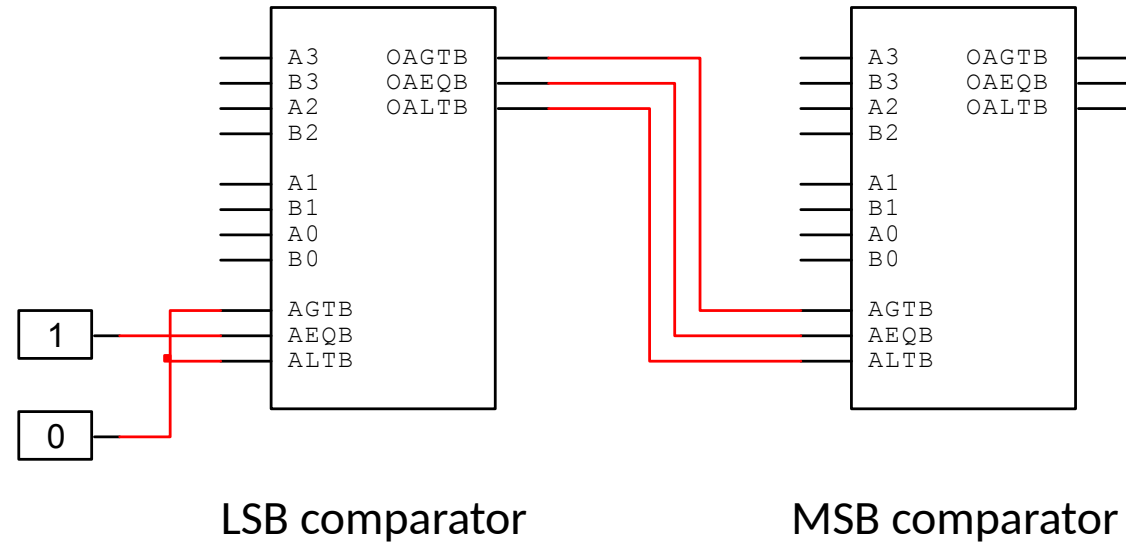 
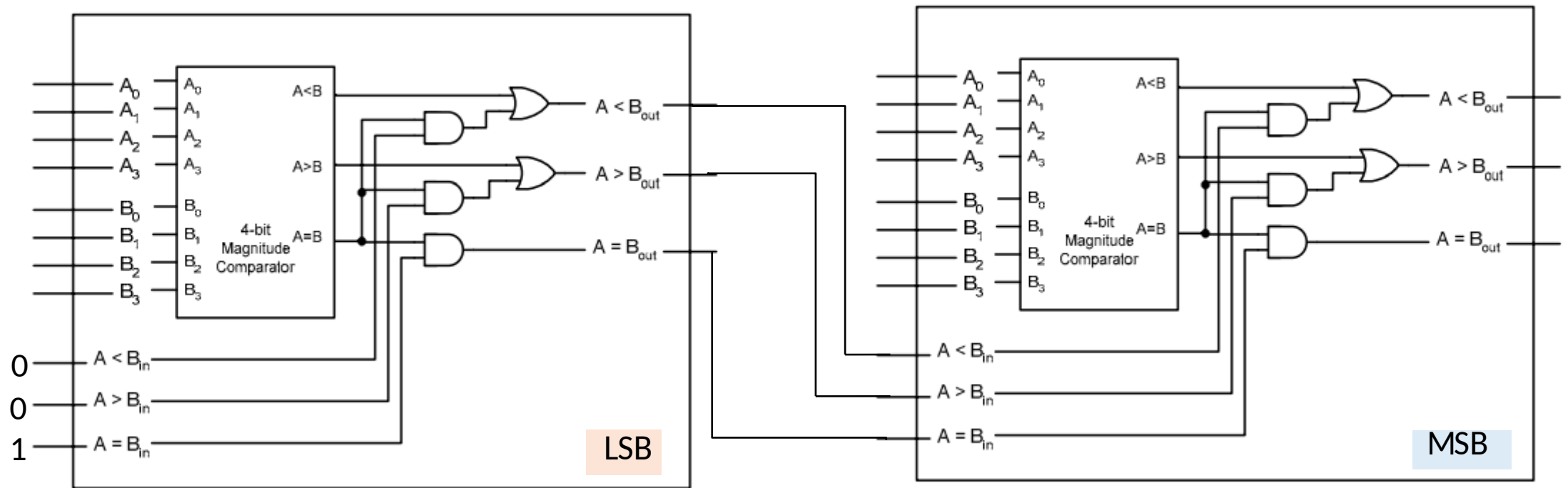
# Expansion Inputs

\* Result of LSB comparator are carried into the MSB comparator



# Unused Inputs

- \* Need two 4-bit comparators to compare 6-bit numbers
- \* Not all inputs will be used, unused inputs are inactive

