

# ESET 219 Homework 3

Name:

Section:

1. Simplify the following Boolean expressions

a.  $\overline{\overline{XY}}$

$$\begin{aligned}(XY)'(Y+X)' \\ X'+Y'(Y'X') \\ X'Y'+X'Y'=X'Y'\end{aligned}$$

b.  $X'YX + XZ$

$$0+XZ=XZ$$

c.  $\overline{A}B\overline{C} + \overline{\overline{A}B\overline{C}} + \overline{A}B\overline{C}D$

$$A'B'C'+(A'B'C)+(A'B'C'D)=A'B'$$


d.  $(\overline{A}B\overline{C} + \overline{A}B\overline{C}D + \overline{A}B\overline{C})$

$$B'C$$

2. For each given schematic


a. Write the Boolean equation for the output F.

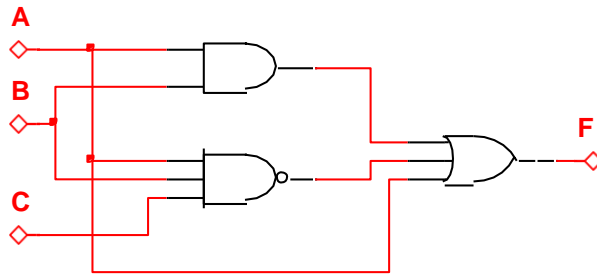b. Use Boolean algebra to simplify F. Draw the simplified circuit schematic




$$A + (ABC)' + AB = F$$
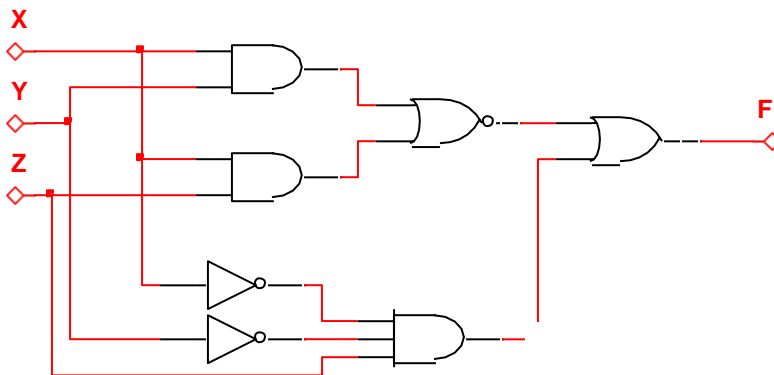
$$\begin{aligned} A + A' + B' + C' + AB \\ 1 + AB + B' + C' \\ 1 = F \end{aligned}$$



$$(XYXZ) + (X'Y'Z) = F$$
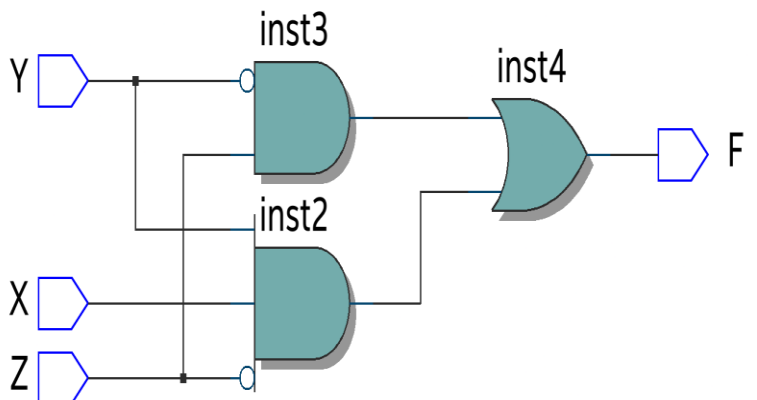
$$\begin{aligned} XY(XZ)' + XZ(XY)' + X'Y'Z \\ XY(X' + Z') + XZ(X' + Y') + X'Y'Z \\ XYZ' + XZY' + X'Y'Z \\ Y'Z(X' + X) + XYZ' \\ XYZ' + Y'Z = F \end{aligned}$$



3. Given the following truth table
- What are all the minterms?
  - What are all the maxterms?
  - Write F as a SOP equation (unsimplified)
  - Use Boolean algebra to simplify F from part c. (must show work for credit)

A	B	C	F		
0	0	0	0	maxterm	$A'B'C'$
0	0	1	1	minterm	$A'B'C$
0	1	0	0	maxterm	$A'BC'$
0	1	1	1	minterm	$A'BC$
1	0	0	0	maxterm	$AB'C'$
1	0	1	0	maxterm	$AB'C$
1	1	0	1	minterm	$ABC'$
1	1	1	1	minterm	$ABC$

$$F = (A'B'C) + (A'BC) + (ABC') + (ABC)$$

$$A'C(B'+B) + AB(C'+C)$$

$$A'C + AB = F$$