

# Frequency Division


Module 16

11/25/2023
 
## 1 Cascading Counters

Cascading a counter effectively makes a larger counter/ increases the MOD of the counter. MOD will determine frequency division, thus having a higher MOD prompts the need of cascading counters.

- The effective MOD of the cascaded counter is the product of all the MODs of each other
- MOD 4 counter cascaded with a MOD 8 will result in a MOD 32 counter.




Cascading asynchronous counters

### 1.1 4 bit Synchronous counter

Cascading synchronous counters require some additional inputs.


- A, B, C, D are initial values to load into the counter → use if the counter starts at a specific value (A is LSB)
- load will place the initial value set by A, B, C, and D inputs into the counter on the next clock edge.
- Clear resets the counter to 0000
- ENP and ENT are enables, both must be HIGH for the counter to work. ENP enables the clock, ENT enables the terminal count (acknowledge when 1111 is reached).

 - \* QA, QB, QC, and QD are the output count with QA being the LSB
- \* ROC is the rollover output that goes high when the counter reaches its terminal count
  - Output will go LOW on next clock pulse after terminal count is reached


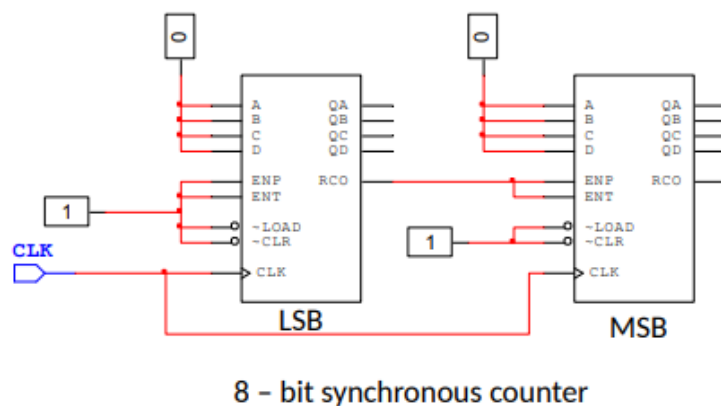
### 1.1.1 Cascading 4-bit Synchronous Counters

- LSB counter is always active
- MSB counter is active only when a terminal count is reached on the LSB counter.




## 1.2 Truncated MOD

\*What if you don't want to use the full MOD of a synchronous counter? (and don't want to create a custom one with state diagrams)

- use the load and initial count inputs to specify the MOD of a counter
- For example, a MOD 16 4 bit counter can be configured into a MOD 4 counter.
- \*Use the RCO output to reload the initial count value
 
## 1.3 Frequency Divider

Any counter will divide the input clock on the output of the flip flops. Thus, the output of a counter can be used as a clock elsewhere in a digital system.



If CLK is 80 Hz, what is the possible clock frequencies that can be used?

The MOD value is


the value a counter can divide frequency of a clock.

- 1KHz clock put into a 25 MOD counter → counter will divide the clock by 25 For every 25 pulses on the clock, 1 pulse is generated
 
### 1.3.1 Potential Problems


\*The output of the RCO (sync.) or the NAND gate (async.) to reset the counter is typically very small in width\*

- Can create problems in using these for a clock signal on another circuit
- clock must have equal time high and low



using a T flip flop will make the output equal HIGH and LOW time

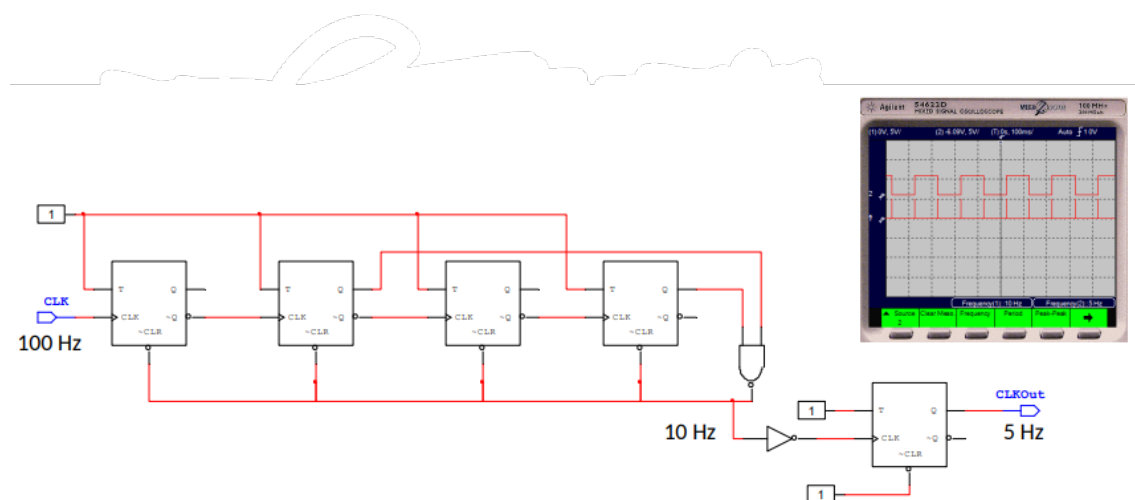- Placing through a fliop flop further divides frquenc by 2



below is an example of a synchronous clock

