

# Counters

---

CASCADING & FREQUENCY DIVISION


# Cascading Counters

---


- \* Counters are cascaded to create larger counters
- \* Used to create higher MOD counters
- \* MOD will be used to determine frequency division

# Cascaded Counters and MOD

 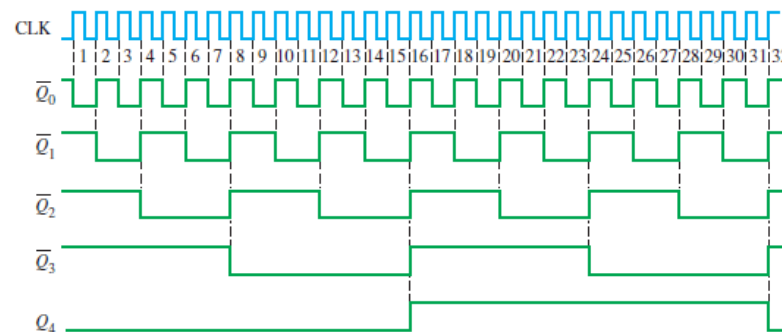- \* The effective MOD of the cascaded counter is the product of all the MODs of each counter
  - A MOD 4 counter cascaded with a MOD 8 counter creates a MOD 32 counter
  - MOD is the total number of counts a counter can count to


 


**FIGURE 9-35** Two cascaded asynchronous counters (all  $J$  and  $K$  inputs are HIGH).

 

# 4 – Bit Synchronous Counter

- \* The 4 – bit synchronous counter in Quartus is representative of a counter IC
- \* Has additional inputs and output
  - ENP, ENT, Load (LDN), Clear (CLR), A, B, C, D
  - RCO




Alternative Schematic Symbol
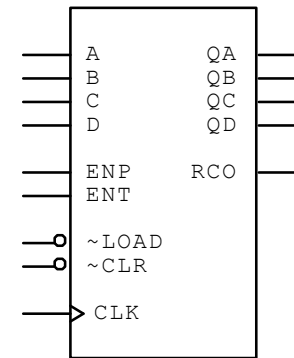
# Inputs

---


- \* A, B, C, D are initial values to load into the counter (1 for each flip flop)
  - Use if the counter starts at a specific value, A is LSB
- \* Load will place the initial value set by A, B, C, and D inputs to the counter on next clock edge
- \* ENP and ENT are enables, both must be HIGH for counter to work
- \* Clear will reset the counter to 0000


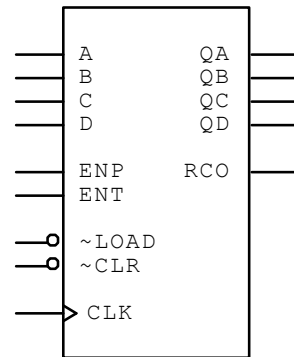
# Outputs


---

- \* QA, QB, QC, and QD are the output count with QA being the LSB
- \* ROC is the rollover output that goes high when the counter reaches its terminal count
  - Output will go LOW on next clock pulse after terminal count is reached


 
# Cascading 4-Bit Synchronous Counters

- \* Need to use the additional inputs and outputs from synchronous counter
  - LSB counter is always active
  - The MSB counter is active only when a terminal count is reached on the LSB counter



8 – bit synchronous counter

# Truncated MOD

---

- \* What if you don't want to use the full MOD of a synchronous counter?  
(and don't want to create a custom one with state diagrams)
- \* Use the load and initial count inputs to specify the MOD of a counter




# Truncated MOD

---

- \* A single 4 – bit counter is MOD 16, how can it be set up to create a MOD 4?
  - What is the difference between max MOD and desired MOD?
  - The difference is the input to the preset inputs
  - Use the RCO output to reload the initial count value
- \* How can a MOD 4 counter be created from a synchronous 4 – bit counter?

# MOD 4 Counter

---

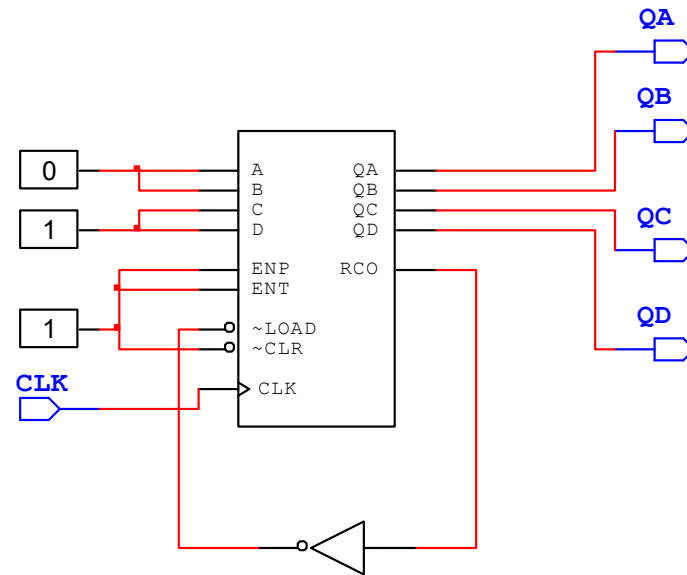


# Example

---

\* How would a synchronous 100 MOD counter be created?


# MOD 100

---

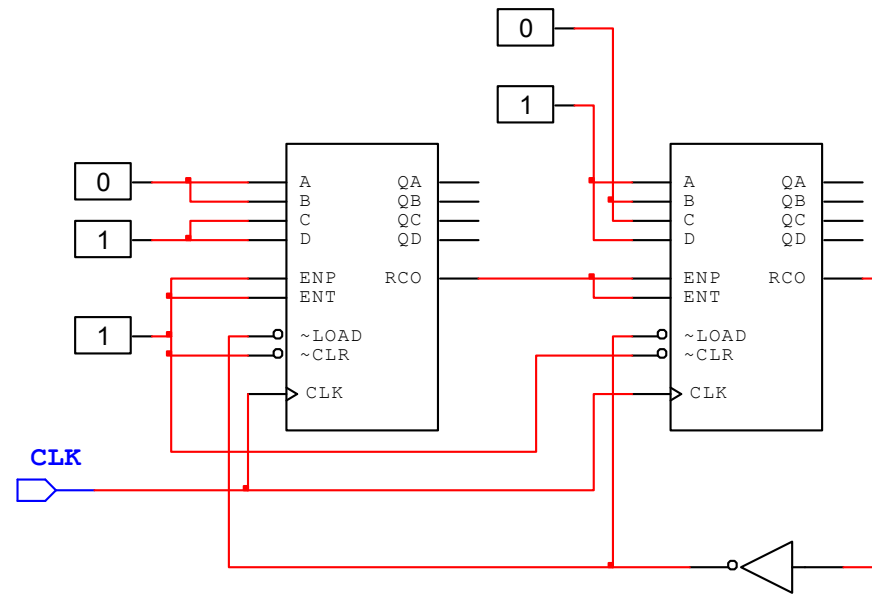
 
# Frequency Divider


- \* Any counter will divide the input clock on the output of the flip flops
- \* Can use the output of counter as another clock elsewhere in digital system



If CLK is 80 Hz, what is the possible clock frequencies that can be used?
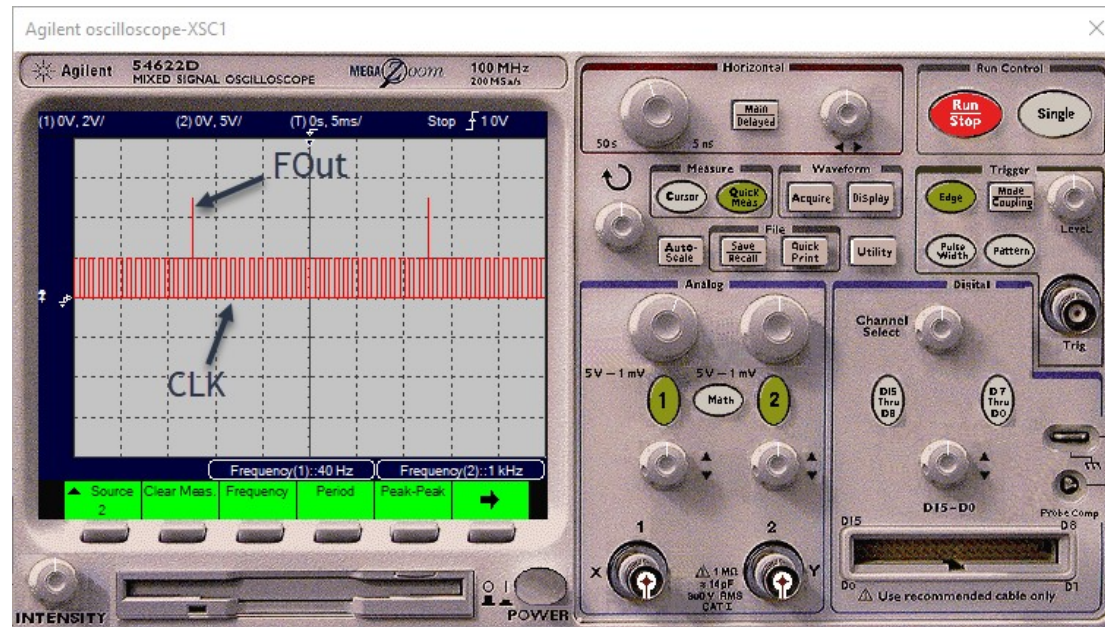
# MOD and Frequency Divider

- \* The MOD value is the value a counter can divide the frequency of a clock
- \* For a 1KHz clock put into a 25 MOD counter, the counter will divide the clock by 25
  - For every 25 pulses on the clock, 1 pulse is generated
  - 40 Hz on signal on output



# Example

---

- \* Create a frequency divider to divide a clock by 20 using T flip flops.

# Example

---

- \* Create a frequency divider to divide a clock by 50 using 4-bit sync. counters



# Potential Problems

---

\*The output of the RCO (sync.) or the NAND gate (async.) to reset the counter is typically very small in width



- Can create problems is using these for a clock signal on another circuit

\* Want a clock to have equal time high and equal time low




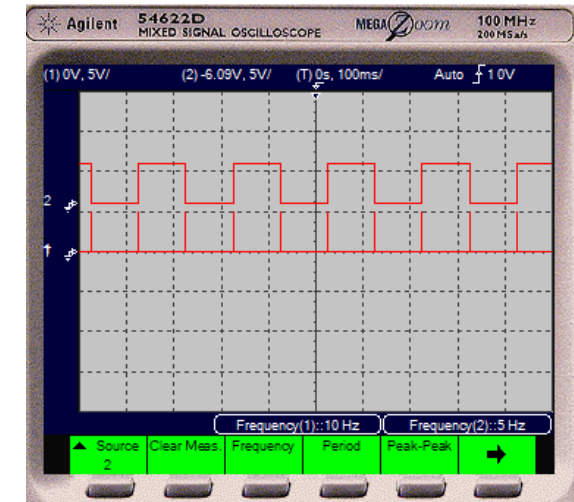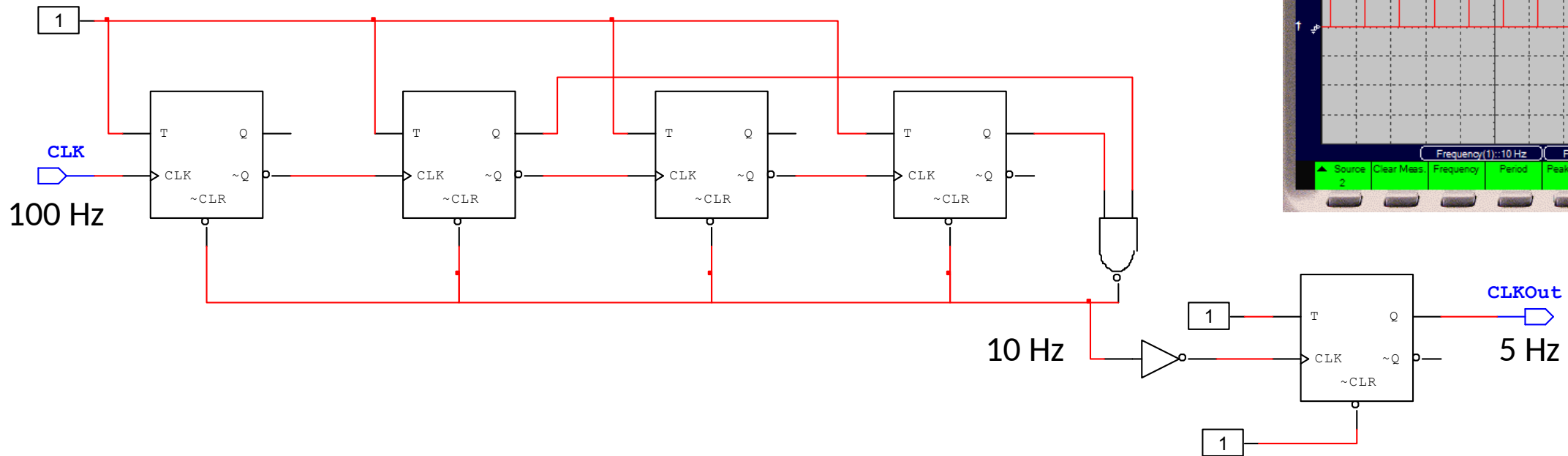
# Creating Clock Signal

- \* Using a T flip flop will make the output equal HIGH and LOW time
  - Placing through a flip flop further divides frequency by 2



# Sync. Example

 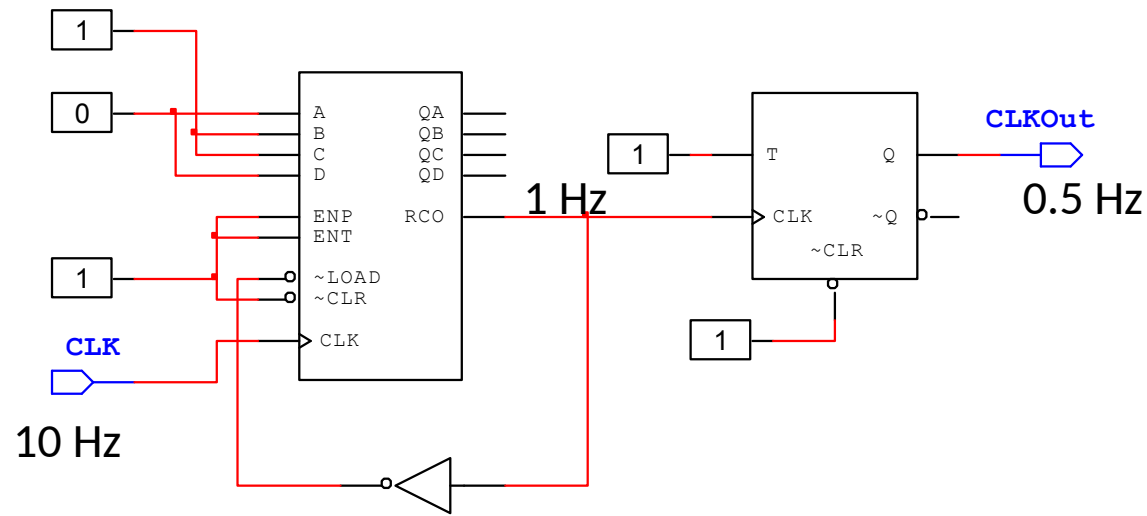


# Example

---

\* Use multiple synchronous 4 – bit counters and other logic elements to create a clock divider of 500. The output clock should have equal HIGH and LOW times.

# Example

 

# Example

---

\* A system has a 1 MHz master clock. A subsystem can only run at a max frequency of 30 kHz. Design the frequency divider for the subsystem clock using a 4-bit synchronous counter. The output should have equal HIGH and LOW time.