

# Basic Logic Design

---

ESET 210

9/13/2023

## 1 Logic Design

Logic gates are put together to create a circuit that performs an operation based on the inputs.

- If the open-door sensor is on AND the security is armed then sound the alarm.
- If launch sequences 1 AND 2 AND 3 are ready OR the principal sequence is ready AND the rocket is fueled, then launch the rocket

Basic logic design using logic gates is thus far known as **combinational logic design**. As soon as the input is changed, the output is changed, and there is no synchronization or clocking involved

### combinational logic

Can have any number of inputs and outputs. These operations are defined by the logic circuits according to their design.

#### Tutorial of such

1. Use a truth table to first define the behaviour
2. How many outputs are needed
3. What combination of inputs will make the outputs **high** or **low**

#### Example

A porch lighting system uses a light sensor to detect if it is dark or light outside. It also contains a motion sensor to detect if someone walks in front of the sensor to turn on a porch light. Also attached to the system is a simple light switch which will turn on and off the porch light.

#### Operation

- If it's dark outside **and** someone crosses the motion sensor, the porch light will come on

- If it's light outside, the motion sensor will not turn on the porch light
- Regardless of if it's light or dark outside, the light switch will turn on the porch light

### **Inputs and Outputs**

#### **Inputs are:**

- light sensor
- Motion sensor
- switch

#### **Outputs are:**

- Porch light