

# Module 3

---

## Logic

9/6/2023

### 1 Binary Codes

Binary Code is how information is represented with binary digits, multiple exist. Codes provide further implementation methods of binary into a digital system.

**Binary Coded Decimal** is code to represent decimal in binary. Each digit is represented by its binary 4-bit equivalent.

Application include numeric LED displays. (BCD is translated digit by digit and the appropriate number is shown )



### 2 Logic

Logic math (**Boolean Algebra**) existed before digital computers. It explained logic, by the means of math, utilizing 2 values (*True or False*).

- As a transistor is a binary output, logic can be implemented
- Basic functions are AND, OR, NOT

- 
- **AND** → All inputs must be true for the expression to be true.  $z = xy, z = x * y$
  - **OR** → Any 1 input can be true for the expression to be true.  $z = x + y$
  - **NOT** → Reverse the expression/scoped output from true to false and vice versa.  $z = x' = \bar{x}$


*Truth Tables of Logical Operations*

AND			OR			NOT	
$x$	$y$	$x \cdot y$	$x$	$y$	$x + y$	$x$	$x'$
0	0	0	0	0	0	0	1
0	1	0	0	1	1	1	0
1	0	0	1	0	1		
1	1	1	1	1	1		
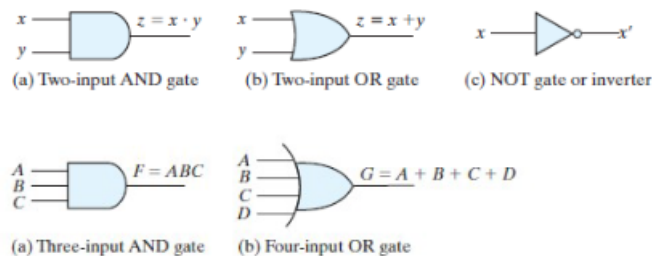
## 2.1 Logic gates

These functions are implemented with logic gates, Electronic device to implement Boolean function.


- These gates have multiple inputs and one output.
- They use specific symbols in their schematic representation


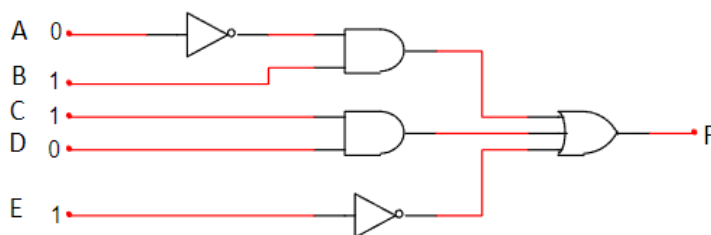
## Boolean Functions

Variables are used to represent inputs and outputs. In a Boolean function, ANDs appear as a product and ORs appear as a sum. NOT is represented with a ' or a bar above the variable.

- In a Boolean function, ANDs appear as a product and ORs appear as a sum. NOT is represented with a ' or a bar above the variable



1. The output of the circuit,  $F$ : 1
2. Circuit as a Boolean expression:  $F = \bar{A}B + CD + \bar{E}$


## Cascading Logic Gates

Logic gates can be cascaded together to create more inputs, for physical logic gates only have a finite amount of inputs.
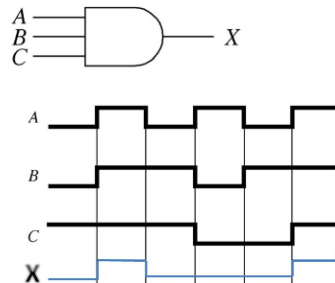
## Timing Diagram

Shows inputs and outputs of a logic circuit over time. output of a logic circuit is assumed to change "instantly".

- Inputs are on the top, outputs are at the bottom, for the sake of readability.



## Truth Tables

describes all of the possible input combinations to generate an output. can be developed from observing a schematic, and conversely, a schematic can be developed using a truth table.


- Left hand side → inputs from MSB to LSB
- Right hand side → outputs from MSB to
- Number of rows =  $2^n$ , where n is the number of inputs

## 3 Additional logic gates
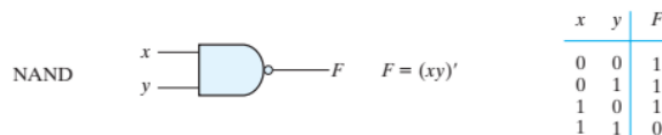
### NAND


$$F = (XY)' = NOT(X \text{ and } Y)$$

**Universal Logic gate:** Any gate can be made with NAND



### NOR


$$F = (X + Y)' = NOT(X \text{ OR } Y)$$

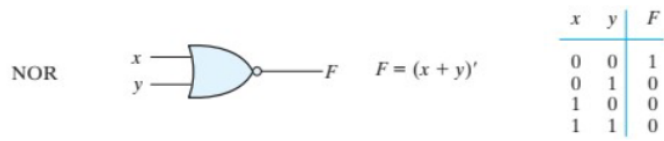

## Exclusively OR (XOR)

$$F = X'Y + XY' = x \text{ or } y \text{ but not both}$$

$$F = X \oplus Y$$

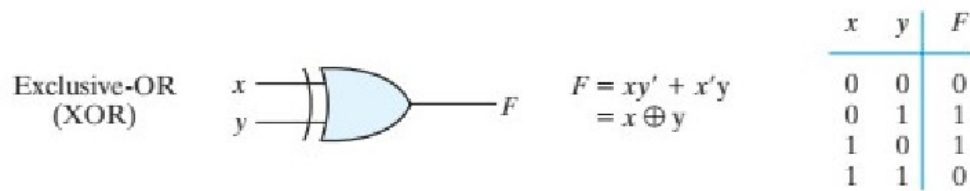

## XNOR

\*Negated xor gate

$$F = XY + X'Y'$$

